

# CS64 Week 6 Lecture 2

Kyle Dewey

# Overview

- More Karnaugh maps
- Exploiting *don't cares* in Karnaugh maps
- Multiplexers

# More Karnaugh Maps

# Another Three Variable Example


$$R = !A!B!C + !A!BC + !ABC + \\ !AB!C + A!B!C + AB!C$$

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

$$R = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}BC + \overline{A}B\overline{C} + A\overline{B}\overline{C} + AB\overline{C}$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 




$$R = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C}$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$R = !A + !C$$

 

# Four Variable Example


$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

---

$$R = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D}$$


		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	1	0	1
 
$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$



$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$


$$R = !B!C$$

 




$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C + !B!D$$

 

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C + !B!D + !AC!D$$

 

# K-Map Rules in Summary (I)

- Groups can contain only 1s
- Only 1s in adjacent groups are allowed (no diagonals)
- The number of 1s in a group must be a power of two (1, 2, 4, 8...)
- The groups must be as large as legally possible

# K-Map Rules in Summary (2)

- All 1s must belong to a group, even if it's a group of one element
- Overlapping groups are permitted
- Wrapping around the map is permitted
- Use the fewest number of groups possible

# Revisiting Problem

$$!A!BC + A!B!C + !ABC + !AB!C + A!BC$$

# Revisiting Problem

$$R = \neg A \neg B C + A \neg B \neg C + \neg A B C + \neg A B \neg C + A \neg B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

# Revisiting Problem

$$R = \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


		BC			
		00	01	11	10
A		-----			
	0	0	1	1	1
	1	1	1	0	0

# Revisiting Problem

$$R = \neg A \neg B C + A \neg B \neg C + \neg A B C + \neg A B \neg C + A \neg B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = \neg A C$$

 




# Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = !AC + A!B$$

 


# Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = !AC + A!B + !AB!C$$

 

# Difference

- Algebraic solution:  $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$
- K-map solution:  $\bar{A}C + A\bar{B} + \bar{A}B\bar{C}$
- Question: why might these differ?

# Difference

- Algebraic solution:  $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$
- K-map solution:  $\bar{A}C + A\bar{B} + \bar{A}B\bar{C}$
- Question: why might these differ?
  - Both are *minimal*, in that they have the fewest number of products possible
  - Can be multiple minimal solutions

# Difference

- Algebraic solution:  $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$
- K-map solution:  $\bar{A}C + A\bar{B} + \bar{A}B\bar{C}$
- Question: why might these differ?
  - Both are *minimal*, in that they have the fewest number of products possible
  - Can be multiple minimal solutions

# Difference

Algebraic solution:  $\neg BC + A\neg B\neg C + \neg AB$

K-map solution:  $\neg AC + A\neg B + \neg AB\neg C$

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	1	0	0

# Difference

Algebraic solution:  $\neg BC + A\neg B\neg C + \neg AB$

K-map solution:  $\neg BC + A\neg B\neg C + \neg AB$

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	1	0	0

# Exploiting *Don't Cares* in K-Maps



# *Don't Cares*

- Occasionally, a circuit's output will be unspecified on a given input
  - Occurs when an input's value is invalid
- In these situations, we say the output is a *don't care*, marked as an  $\times$  in a truth table

# Example: Binary Coded Decimal

- Occasionally, it is convenient to represent decimal numbers directly in binary, using 4-bits per decimal digit
  - For example, a digital display



# Example: Binary Coded Decimal

- Not all binary values map to decimal digits

Binary	Decimal
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7

Binary	Decimal
1000	8
1001	9
1010	X
1011	X
1100	X
1101	X
1110	X
1111	X

# Significance

- Recall that in a K-map, we can only group 1s
- Because the value of a *don't care* is irrelevant, we can treat it as a 1 if it is convenient to do so (or a 0 if that would be more convenient)

# Example

- A circuit that calculates if the binary coded decimal input  $\% 2 == 0$

# Example

- A circuit that calculates if the binary coded decimal input  $\% 2 == 0$

$I_3$	$I_2$	$I_1$	$I_0$	R
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0

$I_3$	$I_2$	$I_1$	$I_0$	R
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

# Example

As a K-map

		$I_1 I_0$			
		00	01	11	10
$I_3 I_2$	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X

# Example

If we don't exploit *don't cares*...

		$I_1 I_0$			
		00	01	11	10
$I_3 I_2$	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X



# Example

If we **do** exploit *don't cares*...

		$I_1 I_0$			
		00	01	11	10
$I_3 I_2$	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X

# Example

If we **do** exploit *don't cares*...

$$R = !I_1!I_0 + I_1I_0$$

		$I_1I_0$			
		00	01	11	10
$I_3I_2$	00	1	0	1	0
	01	1	0	1	0
	11	X	X	X	X
	10	1	0	X	X

# Multiplexers

# Motivation

- At this point, you've seen a lot of straightline circuits
- However, this doesn't quite match up with respect to what a processor does. Why?

# Motivation

- At this point, you've seen a lot of straightline circuits
- However, this doesn't quite match up with respect to what a processor does. Why?
  - We don't always do the same thing - it depends on the instruction
  - What do we need here?

# Motivation

- At this point, you've seen a lot of straightline circuits
- However, this doesn't quite match up with respect to what a processor does. Why?
  - We don't always do the same thing - it depends on the instruction
  - What do we need here?
    - Some form of a conditional

# Conditional

- Assume `selector`, `A`, `B`, and `R` all hold a single bit
- How can we implement this using what we have seen so far? (Hint: what does the truth table look like?)

---

$R = (\text{selector}) ? A : B$

R = (selector) ? A : B

S	A	B	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



$R = (\text{selector}) ? A : B$

S	A	B	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

**Unreduced sum-of-products:**

$$R = \neg S \neg A B + \neg S A B + S \neg A \neg B + S A B$$

$$R = (\text{selector}) ? A : B$$

S	A	B	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

**Unreduced sum-of-products:**

$$R = !S!AB + !SAB + SA!B + SAB$$

**Reduced sum-of-products:**

$$R = !SB + SA$$

# Slight Modification

**Original**

```
R = (selector) ? A : B
```

**Modified**

```
R = (selector) ? doThis() : doThat()
```

# Slight Modification

## Original

$$R = (\text{selector}) ? A : B$$

## Modified

$$R = (\text{selector}) ? \text{doThis}() : \text{doThat}()$$

**Intended semantics: either `doThis()` or `doThat()` is executed. Our formula from before doesn't satisfy this property:**

$$R = !S * \text{doThat}() + S * \text{doThis}()$$

# Slight Modification

## Original

`R = (selector) ? A : B`

## Modified

`R = (selector) ? doThis() : doThat()`

- Fixing this is hard, but possible
- Involves circuitry we'll learn later
- Oddly enough, this isn't as big of a problem as it seems, and it's ironically *faster* than doing just one or the other. Why?

# Slight Modification

## Original

```
R = (selector) ? A : B
```

## Modified


```
R = (selector) ? doThis() : doThat()
```

- Oddly enough, this isn't as big of a problem as it seems, and it's ironically *faster* than doing just one or the other. Why? - branches executed in parallel at the hardware level. Faster because extra circuitry is extra.

# Multiplexer

- Component that does exactly this:

$$R = (\text{selector}) ? A : B$$

 

# Question

- Recall the arithmetic logic unit (ALU), which is used to add, subtract, shift, perform bitwise operations, etc.
- How might a multiplexer be useful for an ALU?

Add Unsigned

addu

R  $R[rd] = R[rs] + R[rt]$

Opcode / Function

0 / 21<sub>hex</sub>

And

and

R  $R[rd] = R[rs] \& R[rt]$

0 / 24<sub>hex</sub>



# Question

- Recall the arithmetic logic unit (ALU), which is used to add, subtract, shift, perform bitwise operations, etc.
- How might a multiplexer be useful for an ALU? - Do all operations at once in parallel, and then use a multiplexer to select the one you want

Add Unsigned

addu

R  $R[rd] = R[rs] + R[rt]$

And

and

R  $R[rd] = R[rs] \& R[rt]$

Opcode / Function


0 / 21<sub>hex</sub>

0 / 24<sub>hex</sub>

# Example

- Let's design a one-bit ALU that can do bitwise AND and bitwise OR
- It has three inputs:  $A$ ,  $B$ , and  $S$ , along with one output  $R$
- $S$  is a code provided indicating which operation to perform; 0 for AND and 1 for OR

# Example

 


# Bigger Multiplexers

- Can have a multiplexer with more than two inputs
- Need multiple select lines in this case
- Question: how many select lines do we need for a 4 input multiplexer?
 
# Bigger Multiplexers

- Can have a multiplexer with more than two inputs
- Need multiple select lines in this case
- Question: how many select lines do we need for a 4 input multiplexer? - 2. Values of different lines essentially encode different binary integers.



# Bigger Multiplexers

- We can build up bigger multiplexers from 2-input multiplexers. How?